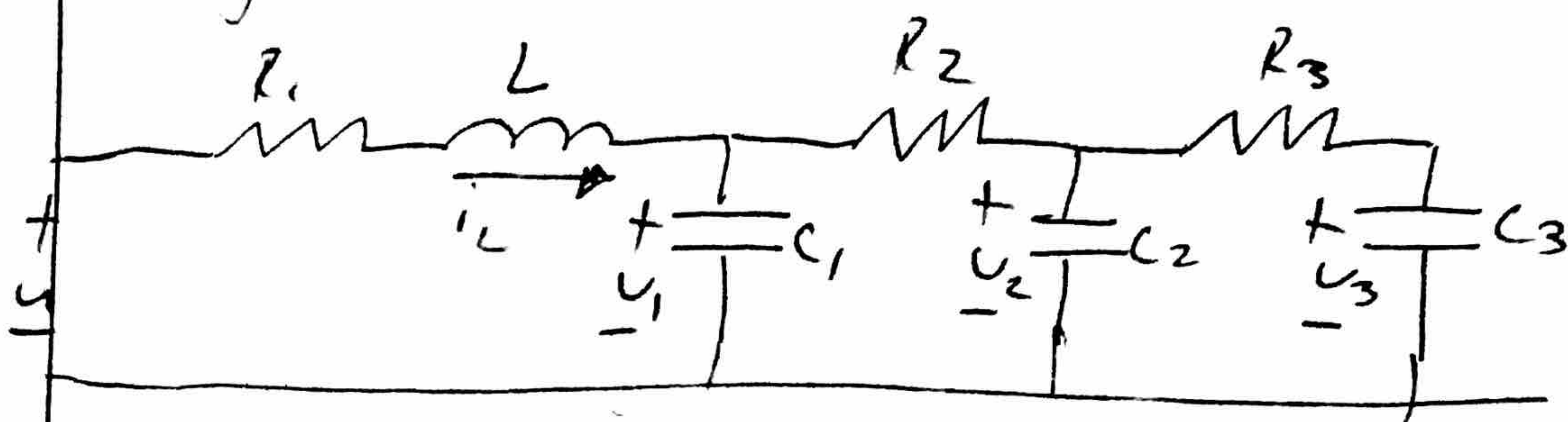


System Simulation Problem #5

Tyler
Matthew
2/13/19



(A) a) $u_1 = x_1$; $u_2 = x_2$; $u_3 = x_3$; $i_L = x_4$

b) $\dot{x}_1 = \frac{1}{C_1} i_L - \frac{x_2 + x_1}{R_2}$

c) $u = R_1 x_4 + L \dot{x}_4 + x_1$

$\frac{x_2 - x_1}{R_2} = \dot{x}_2 C_2 + \frac{-x_3 + x_2}{R_3}$

$\frac{-x_3 + x_2}{R_3} = \dot{x}_3 C_3$

d) $\dot{X} = \begin{pmatrix} \frac{-1}{C_1 R_2} & \frac{1}{C_1 R_2} & 0 & \frac{1}{C_1} \\ \frac{1}{C_2 R_2} & \frac{-1}{C_2 R_2} + \frac{1}{C_2 R_3} & \frac{1}{C_2 R_3} & 0 \\ 0 & \frac{1}{C_3 R_3} & \frac{-1}{C_3 R_3} & 0 \\ \frac{-1}{L} & 0 & 0 & \frac{-R_1}{L} \end{pmatrix} X + \begin{pmatrix} 0 \\ 0 \\ 0 \\ \frac{1}{L} \end{pmatrix} u$

(e) The given matrix $\begin{pmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \\ 0 & 0 & 1 & 0 \end{pmatrix}$ gives each capacitor

voltage (i.e. x_1, x_2, x_3) as an output for the matrix give in part A-d. If we wanted to change our outputs the the matrix would change. For example, x_1 & x_2 as outputs would give the matrix $\begin{pmatrix} 1 & 0 & 0 & 0 \\ 0 & 1 & 0 & 0 \end{pmatrix}$.